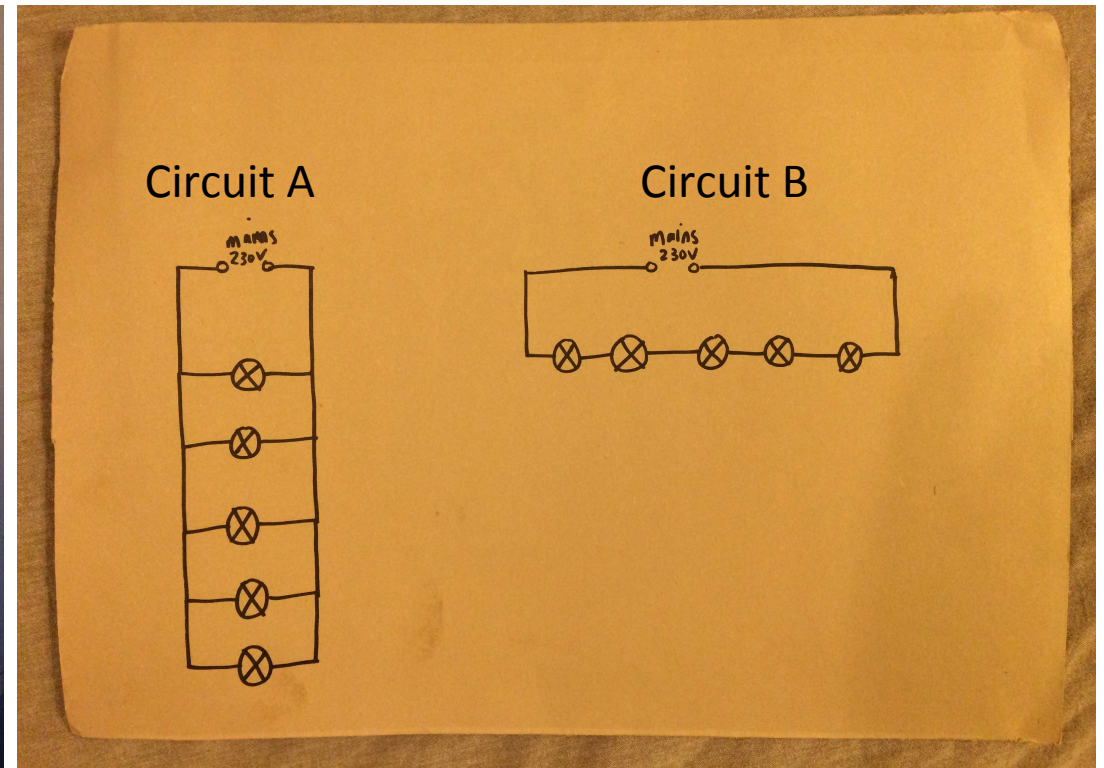


<b>Topic</b>	Series and parallel circuits	<b>Level</b>	Key Stage 3
<b>Outcomes</b>	1. To be able to compare and contrast series and parallel circuits		



**Which circuit will you be using this Christmas?**

1. Will the bulbs be brighter in circuit A or B?
2. If a bulb breaks in circuit A, what will happen to the other lights?
3. If a bulb breaks in circuit B, what will happen to the other lights?